



İzmir Kâtip Çelebi University
Department of Engineering Sciences
Phy102 Physics II
Final Examination
January 14, 2022 11:00 – 12:30
Good Luck!

NAME-SURNAME:

SIGNATURE:

ID:

DEPARTMENT:

INSTRUCTOR:


DURATION: 90 minutes

- ◇ Answer all the questions.
- ◇ Write the solutions explicitly and clearly.
Use the physical terminology.
- ◇ You are allowed to use Formulae Sheet.
- ◇ Calculator is allowed.
- ◇ You are not allowed to use any other electronic equipment in the exam.
- ◇ I declare hereby that I fulfilled the requirements for the attendance according to the University regulations and I accept that my examination will not be valid otherwise.

Question	Grade	Out of
1A		15
1B		15
2		20
3		20
4		20
5		20
TOTAL		110

This page is intentionally left blank. Use the space if needed.

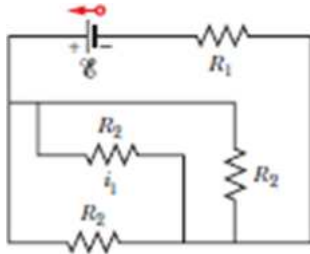1. A) In Figure, $R_1 = 2.0 \Omega$, $R_2 = 6.0 \Omega$, and the ideal battery has emf $\varepsilon = 4.0 \text{ V}$.



- i What are the size and direction (left or right) of current i_1 ?
- ii How much energy is dissipated by all four resistors in 3.00 minutes?

$R_1 = 6 \Omega$
 $R_2 = 18 \Omega$
 $\mathcal{E} = 12 \text{ V}$
 $i_1 = ?$

$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{6} + \frac{1}{6}$ (1.5)
 $R_{eq} = 2 \Omega$ (1.5)
 $i = \frac{V}{R} = \frac{4 \text{ V}}{4 \Omega} = 1 \text{ A}$ (1.5)
 $i_1 = \frac{i}{3} = \frac{1 \text{ A}}{3} = 0.33 \text{ A}$ (Rightward) (1.5)
 $P = i^2 R_{eq} = (1 \text{ A})^2 (4 \Omega) = 4 \text{ W}$ (1.5)
 $P = \frac{\Delta U}{\Delta t} \Rightarrow \Delta U = (4 \text{ W})(180 \text{ sec}) = 720 \text{ J}$ (1.5)

- B) A $15.0 \text{ k}\Omega$ resistor and a capacitor are connected in series and then a 12.0 V potential difference is suddenly applied across them. The potential difference across the capacitor rises to 5.0 V in $1.30 \mu\text{s}$.
- Calculate the time constant of the circuit.
 - Find the capacitance of the capacitor.

Charging capacitor: $q = C \mathcal{E} (1 - e^{-t/RC})$ & $\tau = RC$ (2)

$$V(t) = \mathcal{E} (1 - e^{-t/RC})$$
 (3)

i) $V(t) = \mathcal{E} (1 - e^{-t/RC}) \Rightarrow 5\text{V} = 12\text{V} \left(1 - e^{-\frac{1.3 \times 10^{-6} \text{s}}{15 \times 10^3 \Omega C}}\right)$

$$e^{-1.3 \times 10^{-6} \text{s}/\tau} = 1 - 5/12 \rightarrow \ln e^{-1.3 \times 10^{-6} \text{s}/\tau} = \ln 7/12$$

$$\rightarrow -1.3 \times 10^{-6} \text{s}/\tau = \ln 7/12 \rightarrow \tau = \frac{-1.3 \times 10^{-6} \text{s}}{\ln 7/12} = \frac{-1.3 \times 10^{-6} \text{s}}{-0.54}$$


$$\Rightarrow \tau = 2.41 \mu\text{s}$$
 (2) (3)

ii) $\tau = RC \rightarrow C = \frac{\tau}{R} = \frac{2.41 \times 10^{-6} \text{s}}{15 \times 10^3 \Omega} = 1.61 \times 10^{-10} \text{ F}$

$$= 0.161 \text{ nF}$$

$$= 162 \text{ pF}$$
 (2)

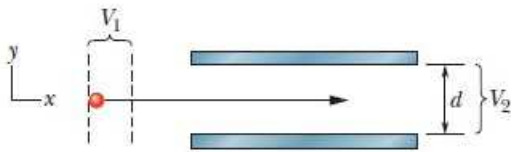2. In Figure, an electron accelerated from rest through potential difference $V_1 = 1.00 \text{ kV}$ enters the gap between two parallel plates having separation $d = 10.0 \text{ mm}$ and potential difference $V_2 = 50 \text{ V}$. The lower plate is at the lower potential. Neglect fringing and assume that the electron's velocity vector is perpendicular to the electric field vector between the plates.



In unit-vector notation, what uniform magnetic field allows the electron to travel in a straight line in the gap?

$V_1 = 1 \text{ kV}$ & $d = 10 \times 10^{-3} \text{ m}$, $V_2 = 50 \text{ V}$, $m_e = 9.11 \times 10^{-31} \text{ kg}$
 higher potential \rightarrow straight line $\Rightarrow |\vec{F}_B| = |\vec{F}_E|$
 $|q|v_z B = |q|E$ (2)
 $\sqrt{\frac{2qV_1}{m_e}} B = \frac{V_2}{d}$ (2)
 $\rightarrow B = \frac{50 \text{ V}}{10 \times 10^{-3} \text{ m}} \sqrt{\frac{9.11 \times 10^{-31} \text{ kg}}{2 \times 1.6 \times 10^{-19} \text{ C} \times 1 \times 10^3 \text{ V}}}$
 $B = 2.67 \times 10^{-4} \text{ T}$
 $\vec{B} = 2.67 \times 10^{-4} \text{ T} (-\hat{y})$ (2) (2)

$\Delta U = qV_1 - 0$ (2)
 $= (1.6 \times 10^{-19} \text{ C}) (1 \times 10^3 \text{ V})$
 $\Delta U = \Delta K = \frac{1}{2} m_e v_z^2$ (2)
 $v_z = Ed$
 $\Rightarrow E = \frac{V_2}{d}$ (2)

(8) lower potential
 $\vec{E} = -\frac{V_2}{d} \hat{y}$
 $\vec{B} = B \hat{y}$

3. A long wire carries a 10 A current from left to right. An electron 1.0 cm above the wire is traveling to the right at a speed of 1.0×10^7 m/s. What are the magnitude and the direction of the magnetic force on the electrons?


$$B = \frac{\mu_0 I}{2\pi d} = \frac{(4\pi \times 10^{-7} \text{ Tm/A}) 10 \text{ A}}{2\pi 1.0 \times 10^{-2} \text{ m}} = 2 \times 10^{-4} \text{ T}$$

$$\vec{F}_B = q \vec{v} \times \vec{B} \Rightarrow |\vec{F}_B| = (1.602 \times 10^{-19} \text{ C})(1.0 \times 10^7 \text{ m/s})(2 \times 10^{-4} \text{ T})$$

$$= 3.2 \times 10^{-16} \text{ N}$$

$$\vec{F}_B = 3.2 \times 10^{-16} \text{ N } \hat{j}$$

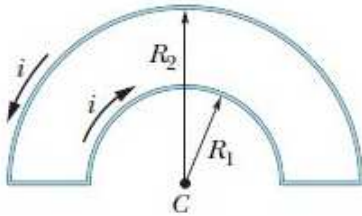4. In Figure, two semicircular arcs have radii $R_2 = 3.9 \text{ cm}$ and $R_1 = 1.575 \text{ cm}$, carry current $i = 0.1405 \text{ A}$, and share the same center of curvature C .



What are the

i magnitude

ii direction (into or out of the page, why?)

of the net magnetic field at C ?

Hint: Use Biot-Savart Law.

$$d\vec{B} = \frac{\mu_0}{4\pi} \frac{i d\vec{s} \times \hat{r}}{r^2}$$
 (Biot-Savart law)

$$dB = \frac{\mu_0}{4\pi} \frac{i ds \sin 90^\circ}{R^2} = \frac{\mu_0}{4\pi} \frac{i ds}{R^2}$$

$$B = \int dB = \frac{\mu_0}{4\pi} i \int \frac{R d\phi}{R^2} = \frac{\mu_0 i}{4\pi R} \phi$$
 (arc angle)

$$B = B_1 + B_2 = \frac{\mu_0 i}{4\pi R_1} \pi - \frac{\mu_0 i}{4\pi R_2} \pi$$

$$= \frac{\mu_0 i \pi}{4\pi} \left(\frac{1}{R_1} - \frac{1}{R_2} \right)$$


$$= \frac{4\pi \times 10^{-7} \text{ Tm/A} \times 0.1405 \text{ A}}{4\pi} \left(\frac{1}{1.575 \times 10^{-2} \text{ m}} - \frac{1}{3.9 \times 10^{-2} \text{ m}} \right)$$

$$= 1.67 \times 10^{-6} \text{ T}$$

Solution
 $\phi = \pi$, $R_2 = 3.9 \times 10^{-2} \text{ m}$
 $R_1 = 1.575 \times 10^{-2} \text{ m}$
 $i = 0.1405 \text{ A}$

ii) into the page \vec{B}_2 \vec{B}_1

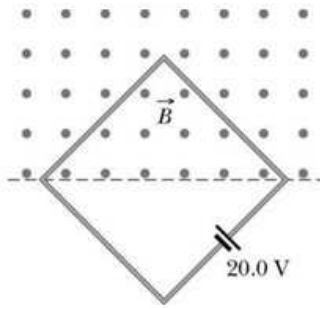5. A square wire loop with 3.00 m sides and resistance $3\ \Omega$ is perpendicular to a uniform magnetic field, with half the area of the loop in the field as shown in figure. The loop contains an ideal battery with emf (ε) 20.0 V . The magnitude of the field varies with time according to $B = 0.0420 - 0.3870t$, with B in teslas and t in second.



- Find the value and direction of the induced ε .
- What is the net emf in the circuit?
- Find the magnitude and the direction of the net current around the loop?

Hint: Magnetic field is decreasing.

$L = 3.00\text{ m}$
 $R = 3\ \Omega$
 $\varepsilon_B = 20.0\text{ V}$
 $B = 0.0420 - 0.3870t$
 $A = L^2/2$

$\varepsilon_i = -\frac{d\Phi_B}{dt} = -\frac{d(LBA)}{dt} = -\frac{L^2}{2} \frac{dB}{dt} = -\frac{L^2}{2} \frac{d(0.0420 - 0.3870t)}{dt}$
 $= -\frac{L^2}{2} (-0.3870\text{ T/s}) = \frac{(3.00\text{ m})^2}{2} (0.3870\text{ T/s})$
 $\varepsilon_i = 1.76\text{ V}$

B is out of page and DECREASING.
 \rightarrow Induced emf should support the external magnetic field \rightarrow CCC: direction of induced emf (current, \Rightarrow some direction with the battery)

$\varepsilon_{\text{total}} = \varepsilon_B + \varepsilon_i = 20.0\text{ V} + 1.76\text{ V} = 21.76\text{ V}$

$i = \frac{V}{R} = \frac{\varepsilon_{\text{total}}}{R} = \frac{21.76\text{ V}}{3\ \Omega} = 7.23\text{ A}$

ii) Current is in the ccw.



İzmir Kâtip Çelebi University
Department of Engineering Sciences
Phy102 Physics II
Final Examination
January 09, 2020 13:30 – 15:30
Good Luck!

NAME-SURNAME:

SIGNATURE:

ID:

DEPARTMENT:

INSTRUCTOR:

DURATION: 120 minutes


- ◇ Answer all the questions.
- ◇ Write the solutions explicitly and clearly.
Use the physical terminology.
- ◇ You are allowed to use Formulae Sheet.
- ◇ Calculator is allowed.
- ◇ You are not allowed to use any other electronic equipment in the exam.
- ◇ I declare hereby that I fulfilled the requirements for the attendance according to the University regulations and I accept that my examination will not be valid otherwise.

Question	Grade	Out of
1A		15
1B		15
2		20
3		20
4		20
5		20
TOTAL		110

This page is intentionally left blank. Use the space if needed.

1. A) The magnitude J of the current density in a certain lab wire with a circular cross section of radius $R=15.00$ mm is given by $J = (6.00 \times 10^7)r^2$, with J in amperes per square meter and radial distance r in meters. What is the current through the outer section bounded by $r=0.200R$ and $r=0.600R$?


$R = 15 \times 10^{-3} \text{ m}$
 $J(r) = 6 \times 10^7 r^2 \text{ A/m}^2$
 $i = ?$ from $r = 0.2R$
 to $r = 0.6R$



$$\begin{aligned}
 i &= \int \vec{J} \cdot d\vec{A} = \int_{0.2R}^{0.6R} 6 \times 10^7 r^2 2\pi r dr \\
 &= 12\pi \times 10^7 \int_{0.2R}^{0.6R} r^3 dr = 12\pi \times 10^7 \left[\frac{r^4}{4} \right]_{0.2R}^{0.6R} \\
 &= 3\pi \times 10^7 [(0.6R)^4 - (0.2R)^4] \\
 &= 3\pi \times 10^7 \times 0.128 R^4 = \underline{0.61 \text{ A}}
 \end{aligned}$$

B) For the circuit shown find

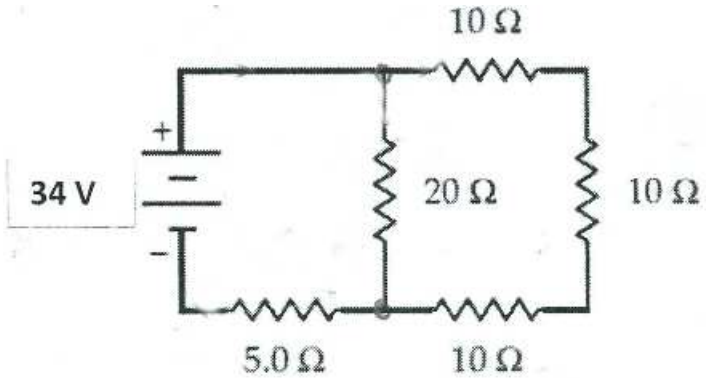- i) the current delivered by the battery,
- ii) the potential difference across the $20\ \Omega$ resistor.



Handwritten solution for problem B:

Step 1: Simplify the parallel resistors. $\frac{1}{R_{eq}} = \frac{1}{20\Omega} + \frac{1}{30\Omega}$
 $R_{eq} = \frac{(30\Omega)(20\Omega)}{20\Omega + 30\Omega} = 12\Omega$ (5)

Step 2: Find the current from the battery. $I = \frac{34V}{17\Omega} = 2A$ (5)


Step 3: Find the potential difference across the 20Ω resistor. $V = IR = 12\Omega \times 2A = 24V$ (5)

Step 4: Find the current through the 20Ω resistor. $I_{20\Omega} = \frac{24V}{20\Omega} = 1.2A$

Step 5: Find the current through the 30Ω resistor. $I_{30\Omega} = \frac{24V}{30\Omega} = 0.8A$

Step 6: Verify the total current. $I = I_1 + I_2$

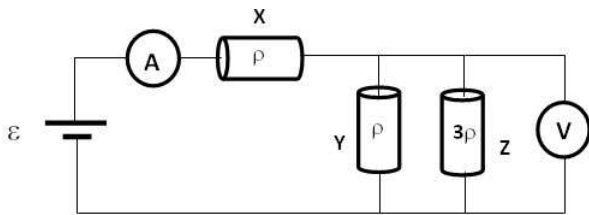2. The circuit containing three cylindrical resistors, namely X, Y and Z, which obey Ohm's Law is shown in the figure below. The resistors which have length of L and cross-sectional area of A are connected to an ideal battery of emf ε . As shown an ammeter is connected in series while voltmeter is connected to ends of resistor Z. The resistors X and Y have a resistivity ρ and the resistor Z has a resistivity 3ρ .



i) Find the current i through the ammeter.

ii) Find the reading of voltmeter. (Hint: Multi-loop circuit. Apply junction and loop rules.)

Express your result in terms of given quantities and constants (ρ, ε, A, L). (Hint: Resistance is related to resistivity.)

i) $\frac{1}{R_{yz}} = \frac{1}{R_y} + \frac{1}{R_z} \Rightarrow R_{yz} = \frac{R_y R_z}{R_y + R_z} \Rightarrow R_{eq} = R_x + R_{yz} = R_x + \frac{R_y R_z}{R_y + R_z}$
 where $R_x = R_y = \rho \frac{L}{A}$ & $R_z = 3\rho \frac{L}{A} \Rightarrow R_{eq} = \rho \frac{L}{A} + \frac{\rho \frac{L}{A} \cdot 3\rho \frac{L}{A}}{\rho \frac{L}{A} + 3\rho \frac{L}{A}}$
 $\Rightarrow R_{eq} = \frac{7\rho L}{4A}$


$i = \frac{\varepsilon}{R_{eq}} = \frac{4\varepsilon A}{7\rho L} = i_x$

ii)

② loop 1: $\varepsilon - i_x R_x - i_y R_y = 0 \Rightarrow i_y = \frac{\varepsilon - i_x R_x}{R_y}$
 ② loop 2: $+i_y R_y - i_z R_z = 0 \Rightarrow i_z = i_y \frac{R_y}{R_z} = \left(\frac{\varepsilon - i_x R_x}{R_y} \right) \frac{R_y}{R_z}$
 $V = i_z R_z = \frac{\varepsilon - i_x R_x}{R_z} R_z = \varepsilon - i_x R_x$
 $= \varepsilon - \left(\frac{4\varepsilon A}{7\rho L} \right) \rho \frac{L}{A} = \varepsilon - \frac{4\varepsilon}{7} = \frac{3\varepsilon}{7}$

3. A proton of kinetic energy 2.10 keV circles in a plane perpendicular to a uniform magnetic field. The orbit radius is 25.0 cm. Find
- the proton's speed,
 - the magnetic field magnitude,
 - the circling frequency,
 - the period of the motion.

proton
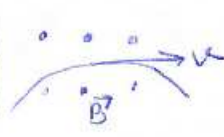
$$\begin{cases}
 m \frac{v^2}{R} = qvB \sin 90 \\
 v = \frac{qRB}{m} \rightsquigarrow R = \frac{mv}{qB}
 \end{cases}$$


i) $\frac{1}{2} m_p v^2 = 2.1 \times 10^3 \text{ eV} \rightsquigarrow v^2 = \frac{2(2.1 \times 10^3 \text{ eV})(1.6 \times 10^{-19} \text{ J/eV})}{1.67 \times 10^{-27} \text{ kg}} = 4.02 \times 10^{11} \text{ m}^2/\text{s}^2$

$\rightsquigarrow v = \boxed{0.634 \times 10^6 \text{ m/s}}$ (3)

ii) $B = \frac{m_p v}{qR} = \frac{(1.67 \times 10^{-27} \text{ kg})(0.634 \times 10^6 \text{ m/s})}{(1.6 \times 10^{-19} \text{ C})(25 \times 10^{-2} \text{ m})} = \boxed{0.027 \text{ T}}$ (3)

iii) $T = \frac{1}{f} = \frac{2\pi R}{v} \rightsquigarrow f = \frac{v}{2\pi R} = \frac{0.634 \times 10^6 \text{ m/s}}{2\pi(25 \times 10^{-2} \text{ m})} = \boxed{0.404 \times 10^6 \text{ Hz}}$ (2)

iv) $T = \frac{1}{f} = \boxed{2.48 \times 10^{-6} \text{ s}}$ (2)

4. A long wire carries a 10 A current from left to right. An electron 1.0 cm above the wire is traveling to the right at a speed of 1.0×10^7 m/s. What are the magnitude and the direction of the magnetic force on the electrons?


$$B = \frac{\mu_0 I}{2\pi d} = \frac{(4\pi \times 10^{-7} \text{ Tm/A}) 10 \text{ A}}{2\pi 1.0 \times 10^{-2} \text{ m}} = 2 \times 10^{-4} \text{ T}$$

$$\vec{F}_B = q \vec{v} \times \vec{B} \Rightarrow |\vec{F}_B| = (1.602 \times 10^{-19} \text{ C})(1.0 \times 10^7 \text{ m/s})(2 \times 10^{-4} \text{ T})$$

$$= 3.2 \times 10^{-16} \text{ N}$$

$$\vec{F}_B = 3.2 \times 10^{-16} \text{ N } \hat{j}$$

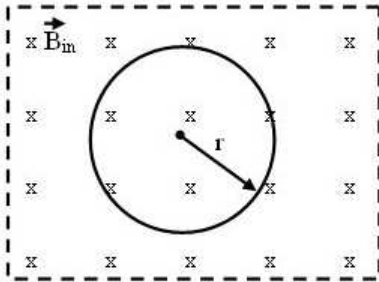5. In figure below, the magnetic flux through the circular loop of radius $r = 2.0 \text{ m}$ increases according to the relation $\Phi_B = 6t^2 + 6t$, where Φ_B is in Webers and t is in seconds.



- Find the magnitude of the induced emf, ξ in the circular loop at $t = 2.0 \text{ s}$.
- What is the magnitude and direction of the induced current in the circular loop at $t = 2.0 \text{ s}$ if the loop has a total resistance of $R = 60 \Omega$?

i) $\Phi_B(t) = 6t^2 + 6t$; increasing flux \Rightarrow induced \mathcal{E}, i should oppose

$$\mathcal{E} = -N \frac{d\Phi_B}{dt} \Rightarrow |\mathcal{E}| = \frac{d(6t^2 + 6t)}{dt} \Big|_{t=2s} = 12t + 6 \Big|_{t=2s}$$

$$\Rightarrow \mathcal{E} \Big|_{t=2s} = \underline{30 \text{ Volt}}$$

ii) $i_{induced} = \frac{\mathcal{E}}{R} = \frac{30 \text{ Volt}}{60 \Omega} = 0.5 \text{ A}$
 direction \rightarrow ccw

The diagram shows the circular loop with induced current $i_{induced}$ flowing counter-clockwise (ccw), indicated by a curved arrow. The induced magnetic field $B_{induced}$ is shown as dots (out of the page) inside the loop.



İzmir Kâtip Çelebi University
Department of Engineering Sciences
Phy102 Physics II
Final Examination
January 09, 2018 14:30 – 16:30
Good Luck!

NAME-SURNAME:

SIGNATURE:

ID:

DEPARTMENT:

DURATION: 120 minutes

- ◇ Answer all the questions.
- ◇ Write the solutions explicitly and clearly.
Use the physical terminology.
- ◇ You are allowed to use Formulae Sheet.
- ◇ Calculator is allowed.
- ◇ You are not allowed to use any other electronic equipment in the exam.
- ◇ I declare hereby that I fulfilled the requirements for the attendance according to the University regulations and I accept that my examination will not be valid otherwise.

Question	Grade	Out of
1A		15
1B		15
2		20
3		20
4		20
5		20
TOTAL		110

This page is intentionally left blank. Use the space if needed.


1. A) A parallel-plate air-filled capacitor has a capacitance of 50 pF .
- If each of its plates has an area of 0.35 m^2 , what is the separation?
 - If the region between the plates is now filled with material having $k=5.6$, what is the capacitance?

i) $C = \epsilon_0 \frac{A}{d} \sim 50 \times 10^{-12} \text{ F} = 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Nm}^2} \frac{0.35 \text{ m}^2}{d}$

$\rightarrow d = \frac{(8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2)(0.35 \text{ m}^2)}{50 \times 10^{-12} \text{ F}} = 0.062 \text{ m}$

ii) $C_1 = kC_0 = (5.6)(50 \times 10^{-12} \text{ F}) = 280 \text{ pF}$

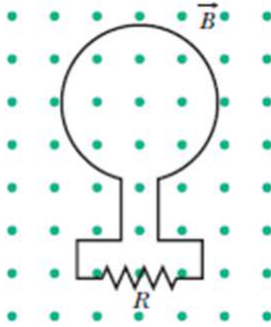- B) In Figure given below, the magnetic flux through the loop increases according to the relation $\Phi_B = 6.0t^2 + 7.0t$, where Φ_B is in miliwebers and t is in seconds.



- i) What is the magnitude of the emf (ϵ) induced in the loop when $t = 2.0$ s?
- ii) Is the direction of the current through R to the right or left?

Increasing magnetic flux \rightarrow induced emf in the loop

$$i) |\epsilon| = \left| \frac{d\Phi_B}{dt} \right| \rightarrow \epsilon = \left. \frac{d(6.0t^2 + 7.0t)}{dt} \right|_{t=2s} = 12t + 7 \Big|_{t=2s}$$


$$\rightarrow \boxed{\epsilon = 31 \text{ mV}}$$

ii) Increasing flux \leftrightarrow induced emf should create a magnetic flux to oppose (to decrease external field)
 To have an inward (induced) B, we should have a clockwise current at the loop.

\rightarrow $\boxed{\text{Left through } R}$


2. The magnitude J of the current density in a certain lab wire with a circular cross section of radius $R=5.00$ mm is given by $J = (2.00 \times 10^7)r^2$, with J in amperes per square meter and radial distance r in meters. What is the current through the outer section bounded by $r=0.800R$ and $r=R$?

$R = 5 \times 10^{-3} \text{ m}$
 $J(r) = 6 \times 10^7 r^2 \text{ A/m}^2$
 $i = ?$ from $r = 0.2R$
 to $r = 0.6R$



$$\begin{aligned}
 i &= \int \vec{J} \cdot d\vec{A} = \int_{0.2R}^{0.6R} 6 \times 10^7 r^2 2\pi r dr \\
 &= 12\pi \times 10^7 \int_{0.2R}^{0.6R} r^3 dr = 12\pi \times 10^7 \left. \frac{r^4}{4} \right|_{0.2R}^{0.6R} \\
 &= 3\pi \times 10^7 [(0.6R)^4 - (0.2R)^4] \\
 &= 3\pi \times 10^7 \times 0.128 R^4 = \underline{\underline{0.61 \text{ A}}}
 \end{aligned}$$

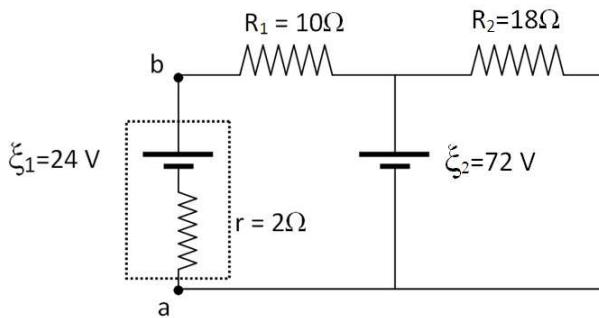3. Consider circuit as shown in figure which consists of two batteries. One of the following batteries has an internal resistance r , while the other battery is an ideal battery. Calculate;



- Currents through each battery,
- Potential difference between points a and b , V_{ab} ,
- Total power supplied by batteries,
- Total power dissipated by resistors.

i) Currents through each battery,

ii) Potential difference between points a and b , V_{ab} ,

iii) Total power supplied by batteries,

iv) Total power dissipated by resistors.

① loop 1: $-i_1 r + \mathcal{E}_1 - i_1 R_1 - \mathcal{E}_2 = 0 \Rightarrow -2i_1 + 24 - 10i_1 - 72 = 0$

② loop 2: $\mathcal{E}_2 - i_3 R_2 = 0 \Rightarrow 72 - 18i_3 = 0 \Rightarrow -12i_3 = -48 \Rightarrow i_3 = 4 \text{ A}$

③ $i_1 + i_2 = i_3 \Rightarrow -4 + i_2 = 4 \Rightarrow i_2 = 8 \text{ A}$

Three unknowns (i_1, i_2, i_3), three equations

$i_1 = -4 \text{ A}$: Through battery 1

$i_2 = 8 \text{ A}$: Through battery 2

$i_3 = 4 \text{ A}$: Through Resistor 3

ii) $V_{ab} = V_b - V_a$

$V_a + i_1 r + \mathcal{E}_1 = V_b$

$V_b - V_a = 4 \text{ A} \cdot 2 \Omega + 24 \text{ V} = 32 \text{ V}$

iii) $P = i \mathcal{E}$

Battery 1: $P_1 = i_1 \mathcal{E}_1 = (-4 \text{ A})(24 \text{ V}) = -96 \text{ W}$

Battery 2: $P_2 = i_2 \mathcal{E}_2 = (8 \text{ A})(72 \text{ V}) = 576 \text{ W}$

$P_1 + P_2 = 480 \text{ W}$

iv) $P = i^2 R$


Resistor 1: $P_1' = i_1^2 R_1 = (4 \text{ A})^2 (10 \Omega) = 160 \text{ W}$

Resistor 2: $P_2' = i_3^2 R_2 = (4 \text{ A})^2 (18 \Omega) = 288 \text{ W}$

Internal Resistor: $P_r' = i_1^2 r = (4 \text{ A})^2 (2 \Omega) = 32 \text{ W}$

$P_1' + P_2' + P_r' = 160 \text{ W} + 288 \text{ W} + 32 \text{ W} = 480 \text{ W}$

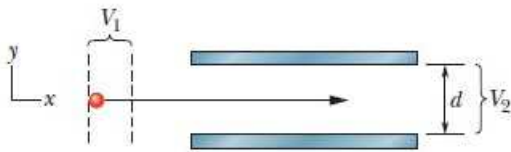4. In Figure, an electron accelerated from rest through potential difference $V_1 = 1.00 \text{ kV}$ enters the gap between two parallel plates having separation $d = 20.0 \text{ mm}$ and potential difference $V_2 = 100 \text{ V}$. The lower plate is at the lower potential. Neglect fringing and assume that the electron's velocity vector is perpendicular to the electric field vector between the plates.




In unit-vector notation, what uniform magnetic field allows the electron to travel in a straight line in the gap?

$V_1 = 1 \text{ kV}$ & $d = 10 \times 10^{-3} \text{ m}$, $V_2 = 50 \text{ V}$, $m_e = 9.11 \times 10^{-31} \text{ kg}$
 higher potential \rightarrow straight line $\Rightarrow |\vec{F}_B| = |\vec{F}_E|$
 $|q|v_z B = |q|E$ (2)
 $\sqrt{\frac{2qV_1}{m_e}} B = \frac{V_2}{d}$ (2)
 $\rightarrow B = \frac{50 \text{ V}}{10 \times 10^{-3} \text{ m}} \sqrt{\frac{9.11 \times 10^{-31} \text{ kg}}{2 \times 1.6 \times 10^{-19} \text{ C} \times 1 \times 10^3 \text{ V}}}$
 $B = 2.67 \times 10^{-4} \text{ T}$
 $\vec{B} = 2.67 \times 10^{-4} \text{ T} (-\hat{y})$ (2) (2)

$\Delta U = qV_1 - 0$ (2)
 $= (1.6 \times 10^{-19} \text{ C}) (1 \times 10^3 \text{ V})$
 $\Delta U = \Delta K = \frac{1}{2} m_e v_z^2$ (2)
 $v_z = Ed$
 $\Rightarrow E = \frac{V_2}{d}$

(8) lower potential (2)
 $\vec{E} = \frac{V_2}{d} \hat{y}$
 $\vec{B} = 2.67 \times 10^{-4} \text{ T} (-\hat{y})$

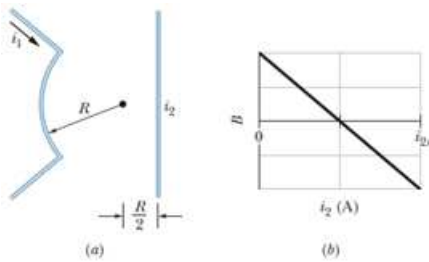5. Figure(a) shows two wires, each carrying a current. Wire 1 consists of a circular arc of radius R and two radial lengths; it carries current $i_1 = 3.0 \text{ A}$ in the direction indicated. Wire 2 is long and straight; it carries a current i_2 that can be varied; and it is at distance $R/2$ from the center of the arc. The net magnetic field B due to the two currents is measured at the center of curvature of the arc.



Figure(b) is a plot of the component of B in the direction perpendicular to the figure as a function of current i_2 . The horizontal scale is set by $i_{2s} = 2.00 \text{ A}$. What is the angle subtended by the arc?

$i_1 = 3 \text{ A}, R$
 $i_2 = \text{variable}, R/2$

net magnetic field at point P
 $B_p = \frac{\mu_0 i_1 \phi}{4\pi R} - \frac{\mu_0 i_2}{2\pi R/2}$

(5) circular arc (out of page) (5) straight wire (into page)

at $i_2 = 1 \text{ A} \Rightarrow B_p = 0 \Rightarrow \frac{\mu_0 3 \text{ A}}{4\pi R} \phi = \frac{\mu_0 1 \text{ A}}{\pi R}$

$\Rightarrow \phi = \frac{4}{3} \text{ radians} = 76.4^\circ$ (2)
 (3.14 rad $\Rightarrow 180^\circ$) (3)