



İzmir Kâtip Çelebi University
Department of Engineering Sciences
Phy102 Physics II
Final Examination
January 09, 2023 17:00 – 18:30
Good Luck!

NAME-SURNAME:

SIGNATURE:

ID:

DEPARTMENT:

INSTRUCTOR:


DURATION: 90 minutes

- ◇ Answer all the questions.
- ◇ Write the solutions explicitly and clearly.
Use the physical terminology.
- ◇ You are allowed to use Formulae Sheet.
- ◇ Calculator is allowed.
- ◇ You are not allowed to use any other electronic equipment in the exam.
- ◇ I declare hereby that I fulfilled the requirements for the attendance according to the University regulations and I accept that my examination will not be valid otherwise.

Question	Grade	Out of
1A		15
1B		15
2		20
3		20
4		20
5		20
TOTAL		110

This page is intentionally left blank. Use the space if needed.

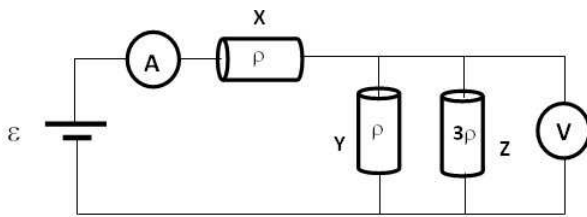1. A) The circuit containing three cylindrical resistors, namely X, Y and Z, which obey Ohm's Law is shown in the figure below. The resistors which have length of L and cross-sectional area of A are connected to an ideal battery of emf ε . As shown an ammeter is connected in series while voltmeter is connected to ends of resistor Z. The resistors X and Y have a resistivity ρ and the resistor Z has a resistivity 3ρ .




i) Find the current i through the ammeter.

ii) Find the reading of voltmeter.

Express your result in terms of given quantities and constants (ε , A , ρ , L). (**Hint:** Resistance is related to resistivity; $R = \rho \frac{L}{A}$)

i) $\frac{1}{R_{yz}} = \frac{1}{R_y} + \frac{1}{R_z} \rightarrow R_{yz} = \frac{R_y R_z}{R_y + R_z} \Rightarrow R_{eq} = R_x + R_{yz} = R_x + \frac{R_y R_z}{R_y + R_z}$
 where $R_x = R_y = \rho \frac{L}{A}$ & $R_z = 3\rho \frac{L}{A} \Rightarrow R_{eq} = \rho \frac{L}{A} + \frac{\rho \frac{L}{A} \cdot 3\rho \frac{L}{A}}{\rho \frac{L}{A} + 3\rho \frac{L}{A}} = \frac{7}{4} \rho \frac{L}{A}$ (2)

$\varepsilon = i R_{eq} \rightarrow i = \frac{\varepsilon}{R_{eq}} = \frac{4 \varepsilon A}{7 \rho L} = i_x \rightarrow i_x = i_y + i_z$ (1)

ii)  Loop 1: $\varepsilon - i_x R_x - i_y R_y = 0 \rightarrow i_y = \frac{\varepsilon - i_x R_x}{R_y}$ (2)
 Loop 2: $i_y R_y - i_z R_z = 0 \rightarrow i_z = i_y \frac{R_y}{R_z}$ (2)

$\Rightarrow i_y = \frac{\varepsilon - i_x R_x}{R_y}$ & $i_z = \left(\frac{\varepsilon - i_x R_x}{R_y} \right) \frac{R_y}{R_z} = \frac{\varepsilon - i_x R_x}{R_z}$ (1)


$\Rightarrow V = i_z R_z = \left(\frac{\varepsilon - i_x R_x}{R_z} \right) R_z = \varepsilon - i_x R_x = \varepsilon - \left(\frac{4 \varepsilon A}{7 \rho L} \right) \rho \frac{L}{A} = \varepsilon - \frac{4 \varepsilon}{7}$

$V = \frac{3 \varepsilon}{7}$ (1)

- B) What uniform magnetic field, applied perpendicular to a beam of electrons moving at $1.30 \times 10^6 \text{ m/s}$, is required to make the electrons travel in a circular arc of radius of 0.35 m? (Hint: Centripetal Force; $F_c = m \frac{v^2}{R}$)

$$\begin{aligned}
 v &= 1.3 \times 10^6 \text{ m/s} & F_c &= m \frac{v^2}{R} \text{ \& } F_B = |q|vB \sin \theta \\
 R &= 0.35 \text{ m} \\
 e &= 1.602 \times 10^{-19} \text{ C} (\equiv |q|) & |q|vB \sin 90^\circ &= m_e v^2 / R \quad (S) \\
 m_e &= 9.109 \times 10^{-31} \text{ kg} & \Rightarrow B &= \frac{m_e v}{e R} \quad (S) \\
 B &=? & &= \frac{(9.109 \times 10^{-31} \text{ kg})(1.3 \times 10^6 \text{ m/s})}{(1.602 \times 10^{-19} \text{ C})(0.35 \text{ m})} \\
 & & &= \boxed{2.11 \times 10^{-5} \text{ T}} \quad (S)
 \end{aligned}$$

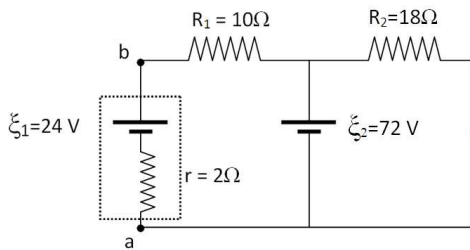2. Consider circuit as shown in figure which consists of two batteries. One of the following batteries has an internal resistance r , while the other battery is an ideal battery.



Calculate;

- Currents through each battery,
- Total power dissipated by resistors.
- Potential difference between points a and b , V_{ab} ,

i) Currents through each battery,

ii) Potential difference between points a and b , V_{ab} ,

iii) Total power supplied by batteries,

iv) Total power dissipated by resistors.

① loop 1: $-i_1 r + \mathcal{E}_1 - i_1 R_1 - \mathcal{E}_2 = 0 \Rightarrow -2i_1 + 24 - 10i_1 - 72 = 0$

② loop 2: $\mathcal{E}_2 - i_3 R_2 = 0 \Rightarrow 72 - 18i_3 = 0 \Rightarrow -12i_3 = -48$

③ $i_1 + i_2 = i_3 \Rightarrow -4A + i_2 = 4A \Rightarrow i_2 = 8A$

Three unknowns (i_1, i_2, i_3), three equations

$i_1 = -4A$: Through battery 1
 $i_2 = 8A$: Through battery 2
 $i_3 = 4A$: Through Resistor 3

ii) $V_{ab} = V_b - V_a$

$V_a + i_1 r + \mathcal{E}_1 = V_b$

$V_b - V_a = 4A \cdot 2\Omega + 24V = 32V$

iii) $P = i \mathcal{E}$

Battery 1: $P_1 = i_1 \mathcal{E}_1 = (4A)(24V) = -96W$

Battery 2: $P_2 = i_2 \mathcal{E}_2 = (8A)(72V) = 576W$

$P_1 + P_2 = 480W$

iv) $P = i^2 R$


Resistor 1: $P_1' = i_1^2 R_1 = (4A)^2 (10\Omega) = 160W$

Resistor 2: $P_2' = i_3^2 R_2 = (4A)^2 (18\Omega) = 288W$

Internal Resistor: $P_r' = i_1^2 r = (4A)^2 (2\Omega) = 32W$

$P_1' + P_2' + P_r' = 480W$

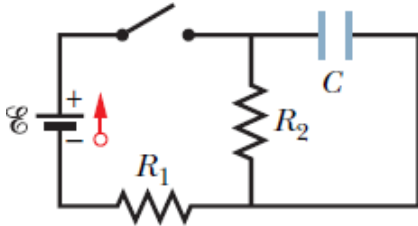3. In Figure given below, $R_1 = 8.0 \times 10^3 \Omega$, $R_2 = 10.0 \times 10^3 \Omega$, $C = 6 \times 10^{-7} F$, and the ideal battery has emf $\epsilon = 12.0 V$. First, the switch is closed a long time so that the steady state is reached. Then the switch is opened at time $t = 0$.



What is the current in resistor 2 at $t = 2.00 \times 10^{-3} s$?

$R_1 = 8 \text{ k}\Omega$
 $R_2 = 10 \text{ k}\Omega$
 $C = 0.6 \mu\text{F}$
 $\mathcal{E} = 12 \text{ V}$

initially, C acts as a connecting wire ①
 after a long time, C acts as a broken wire ②

① Charging stage ② fully charged

$\Rightarrow V_C = V_{R_2} = iR_2$
 $i = \frac{\mathcal{E}}{R_1 + R_2}$ ②


$\rightarrow V_{R_2} = \left(\frac{\mathcal{E}}{R_1 + R_2}\right) R_2 = \frac{12 \text{ V}}{(8 \text{ k}\Omega + 10 \text{ k}\Omega)} \cdot 10 \text{ k}\Omega = \frac{20 \text{ V}}{3} (= V_C)$ when fully charged ②

③ switch is opened $\rightarrow t = 0$ & $V_C = V_0 = \frac{20}{3} \text{ V}$ ②
 discharging through R_2 , $V = V_0 \exp(-t/RC)$ ③

$\rightarrow V = \left(\frac{20}{3} \text{ V}\right) \exp\left(-\frac{2 \text{ ms}}{(10 \text{ k}\Omega)(0.6 \mu\text{F})}\right) = \left(\frac{20}{3} \text{ V}\right) \exp\left(-\frac{2 \times 10^{-3} \text{ s}}{10 \times 10^3 \Omega \cdot 0.6 \times 10^{-6} \text{ F}}\right)$

$V(t = 2 \text{ ms}) = 4.78 \text{ V}$ ② $\rightarrow i_{R_2} = \frac{V}{R_2} = \frac{4.78 \text{ V}}{10 \text{ k}\Omega} = 4.77 \times 10^{-4} \text{ A}$ ② ①

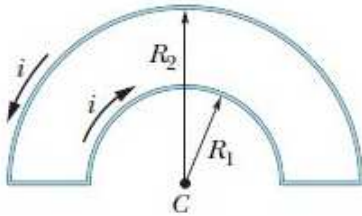4. In Figure, two semicircular arcs have radii $R_2 = 2.6 \text{ cm}$ and $R_1 = 1.05 \text{ cm}$, carry current $i = 0.0937 \text{ A}$, and share the same center of curvature C .



What are the

i magnitude

ii direction (into or out of the page, why?)

of the net magnetic field at C ?

Hint: Use Biot-Savart Law.

Biot-Savart law: $d\vec{B} = \frac{\mu_0}{4\pi} \frac{i d\vec{s} \times \hat{r}}{r^2} \rightarrow$

$$dB = \frac{\mu_0}{4\pi} \frac{i ds \sin 90^\circ}{R^2} = \frac{\mu_0}{4\pi} \frac{i ds}{R^2} \quad \left\{ \begin{array}{l} \text{where} \\ ds = R d\phi \end{array} \right\} \rightarrow B = \int dB$$

$$\rightarrow B = \frac{\mu_0}{4\pi} i \int_0^\phi \frac{R d\theta}{R^2} = \frac{\mu_0 i}{4\pi R} \phi \quad \left\{ \begin{array}{l} \text{where} \\ \phi \text{ is arc angle} \end{array} \right.$$

$R_1 = 1.05 \times 10^{-2} \text{ m}$
 $R_2 = 2.6 \times 10^{-2} \text{ m}$
 $i = 0.0937 \text{ A}$
 $\phi = 180^\circ \equiv \pi$

i) $B = B_1 + B_2 = \frac{\mu_0 i}{4\pi} \left(\frac{1}{R_1} - \frac{1}{R_2} \right) \pi$ (4)


$$\rightarrow B = \frac{4\pi \times 10^{-7} \text{ Tm/A} \cdot 0.0937 \text{ A}}{4\pi} \left(\frac{1}{1.05 \times 10^{-2} \text{ m}} - \frac{1}{2.6 \times 10^{-2} \text{ m}} \right) \pi$$

$$= 1.67 \times 10^{-6} \text{ T} \quad (2)$$

ii) into the page (4)

B_1 (into the page) & $|B_1| > |B_2|$
 B_2 (out of the page)

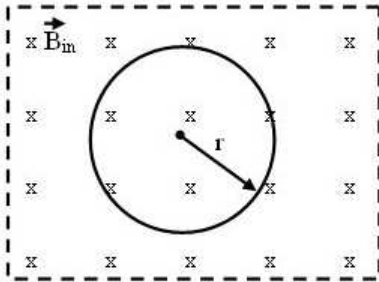5. In figure below, the magnetic flux through the circular loop of radius $r = 2.0 \text{ m}$ increases according to the relation $\Phi_B = 3t^2 + 3t$, where Φ_B is in Webers and t is in seconds.



- Find the magnitude of the induced emf, ξ in the circular loop at $t = 2.0 \text{ s}$.
- What is the magnitude and direction of the induced current in the circular loop at $t = 2.0 \text{ s}$ if the loop has a total resistance of $R = 30 \Omega$?

i) $\Phi_B(t) = 3t^2 + 3t$: increasing flux \Rightarrow induced \mathcal{E}, i should oppose

$\mathcal{E} = -N \frac{d\Phi_B}{dt} \xrightarrow{(5)} |\mathcal{E}| = \left. \frac{d(3t^2 + 3t)}{dt} \right|_{t=2s} = 6t + 3 = 15 \text{ V} \quad (5)$

ii) $i = \frac{\mathcal{E}}{R} = \frac{15 \text{ V}}{30 \Omega} = 0.5 \text{ A} \quad (2)$

$\vec{B}_{applied} \otimes \sim$ into the page (2)
 $\vec{B}_{induced} \odot \leftarrow$ since it should oppose
 by Right Hand Rule \sim direction of induced current is ccw (3)

The diagram shows the circular loop with induced current flowing counter-clockwise (ccw) and induced magnetic field $\vec{B}_{induced}$ directed out of the page, represented by 'o' marks.