



İzmir Kâtip Çelebi University
Department of Engineering Sciences
Phy102 Physics II
Final Examination
June 08, 2026 10:20 – 11:50
Good Luck!

NAME-SURNAME:

SIGNATURE:

◇ I declare hereby that I fulfilled the requirements for the attendance according to the University regulations and I accept that my examination will not be valid otherwise.

ID:

DEPARTMENT:

INSTRUCTOR:

DURATION: 90 minutes

- ◇ Answer all the questions.
- ◇ Write the solutions explicitly and clearly. Use the physical terminology.
- ◇ You are allowed to use Formulae Sheet.
- ◇ Calculator is allowed.
- ◇ You are not allowed to use any other electronic equipment in the exam.

Question	Grade	Out of
1A		15
1B		15
2		20
3		20
4		15
5		15
TOTAL		100

This page is intentionally left blank. Use the space if needed.

1. A) A 24.0 m length of 2.0 mm diameter cylindrical conducting wire carries a 140 A current when 28.0 V is applied to its ends.
- Calculate the resistance R and resistivity ρ of the conducting wire.
 - Find the current density J and electric field E inside the conducting wire.
 - If the current is maintained in the conductor for 3 hours, calculate the dissipated energy in the conducting wire.

$$i) \quad R = \frac{V}{I} \quad \& \quad R = \rho \frac{L}{A} \quad \leadsto \quad \rho = \frac{A}{L} R, \quad A = \pi r^2$$

$$R = \frac{28V}{140A} = 0.2 \Omega$$

$$= \frac{\pi (2 \times 10^{-3} m / 2)^2}{24m} 0.2 \Omega$$

$$= 2.6 \times 10^{-8} \Omega m$$


$$ii) \quad J = \frac{I}{A} = \frac{140A}{\pi (10^{-3} m)^2} = 4.5 \times 10^7 A/m^2$$

$$E = \rho J = (2.6 \times 10^{-8} \Omega m)(4.5 \times 10^7 A/m^2) = 1.2 V/m$$

$$iii) \quad \frac{\Delta U}{\Delta t} = P = i^2 R \quad \leadsto \quad \Delta U = i^2 R \Delta t$$

$$\leadsto \Delta U = (140A)^2 (0.2 \Omega) (3 \times 60 \times 60 s) = 4.2 \times 10^7 J$$

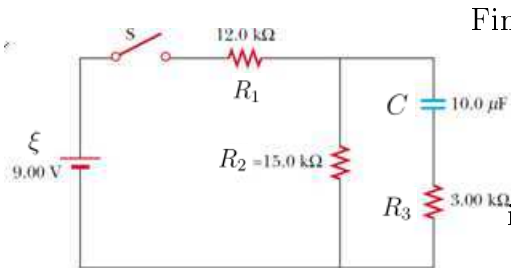
- B) A circuit is assembled as shown at the figure. If $R_1 = 12 \text{ k}\Omega$, $R_2 = 15 \text{ k}\Omega$, $R_3 = 3 \text{ k}\Omega$, $C = 10 \text{ }\mu\text{F}$ and $\xi = 9 \text{ V}$. Suppose the switch has been closed for a time interval sufficiently long for the capacitor to become fully charged.



Find

- the steady-state current in each resistor
- the charge Q on the capacitor
- The switch is now opened at $t=0$. Write an equation for the current in R_2 as a function of time.

sufficiently long time interval \rightarrow C becomes broken wire (2)
 (steady-state)
 i) $I_{R_3} = 0$ since C is acting as broken wire
 $I_{R_1} = I_{R_2} = I = \frac{\xi}{R_1 + R_2} = \frac{9\text{V}}{(12\text{k}\Omega + 15\text{k}\Omega)} = 333 \mu\text{A}$ (1)(1)
 ii) $C = \frac{Q}{V} \sim Q = CV = C(IR_2) = (10\mu\text{F})(333\mu\text{A})(15\text{k}\Omega) = 50 \mu\text{C}$ (1)(1)
 iii) switch is opened, C behaves as a battery; $(\Delta V)_C$
 $t=0$

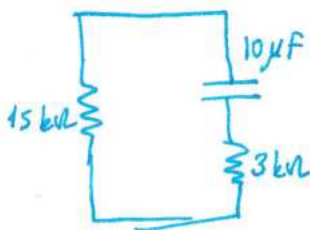


$$I_{t=0} = \frac{(\Delta V)_C}{R_2 + R_3} = \frac{IR_2}{R_2 + R_3} = \frac{(333\mu\text{A})(15\text{k}\Omega)}{(15\text{k}\Omega + 3\text{k}\Omega)} = 278 \mu\text{A} = I_2$$

$$\text{Time Constant: } \tau = (R_2 + R_3)C = (18\text{k}\Omega)(10\mu\text{F}) = 0.180\text{s}$$

$$I_{R_2} = I_2 e^{-t/\tau} = (278 \mu\text{A}) e^{-t/0.180\text{s}} \text{ for } t > 0$$

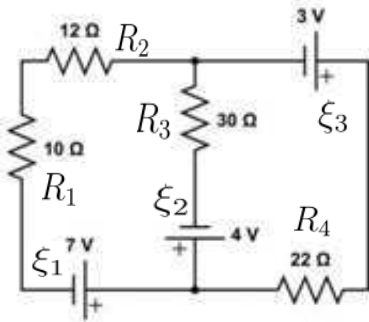2. A circuit is assembled as shown at the figure. If $R_1 = 10 \Omega$, $R_2 = 12 \Omega$, $R_3 = 30 \Omega$, $R_4 = 22 \Omega$, $\xi_1 = 7 \text{ V}$, $\xi_2 = 4 \text{ V}$, and $\xi_3 = 3 \text{ V}$;



- i What is the magnitude of the current through the 30Ω resistor?
 ii How much power is drawn by the 7 V battery?


Handwritten solution showing circuit analysis:

$22i_4 + 30i_2 = 3$
 $-30i_2 - 22i_3 = 1$
 $22i_4 + 30(4 + i_3) = 3$
 $-30(4 + i_3) - 22i_3 = 1$
 $52i_4 + 30i_3 = 3$
 $-30i_4 - 52i_3 = 1$
 $52i_4 + 30\left(\frac{-1 - 30i_4}{-52}\right) = 3$
 $i_4 = 0.103 \text{ A}$
 $i_3 = \frac{-1}{52} - \frac{30}{52}i_4 = -0.078 \text{ A}$
 $i_2 = 0.0244 \text{ A}$ (i)

Junction rule: $i_4 + i_3 = i_2$ (3)
 Loop 1: $-12i_1 - 10i_1 + 7 - 4 - 30i_2 = 0$ (3)
 Loop 2: $3 - 22i_3 - 4 - 30i_2 = 0$ (3)

ii) $P = iV = i_1 7 \text{ V}$
 $= (0.103 \text{ A})(7 \text{ V}) = 0.72 \text{ W}$

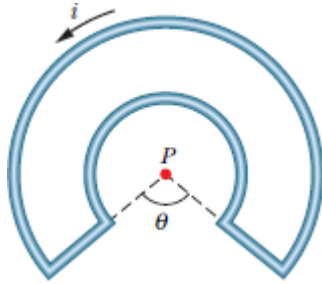3. In figure given below, a closed loop carries current $i = 200 \text{ mA}$. The loop consists of two radial straight wires and two concentric circular arcs of radii 2.00 m and 4.00 m . The angle θ is $\pi/4 \text{ rad}$.



What are the magnitude and direction (into or out of the page) of the *net magnetic field* at the center of curvature P?

$i = 200 \text{ mA} = 0.2 \text{ A}$
 $R_1 = 4 \text{ m}$ & $R_2 = 2 \text{ m}$

$$\vec{B}_{\text{net},P} = \vec{B}_1 + \vec{B}_2 + \vec{B}_3 + \vec{B}_4$$

$$|\vec{B}_2| = 0, |\vec{B}_4| = 0 \quad \left\{ \begin{array}{l} \vec{i} \parallel d\vec{s} \\ \text{into page} \end{array} \right.$$

$$B = \frac{\mu_0 i}{4\pi r} \phi \quad (3)$$

$$\phi = 2\pi - \frac{\pi}{4} = \frac{7\pi}{4} \quad (3)$$

$$B_1 = \frac{\mu_0 i}{4\pi R_1} \phi \quad (3) \rightarrow B_1 = \frac{\mu_0 i}{4\pi R_1} \frac{7\pi}{4} \quad (2)$$

$$B_3 = \frac{\mu_0 i}{4\pi R_2} \phi \quad (3) \rightarrow B_3 = \frac{\mu_0 i}{4\pi R_2} \frac{7\pi}{4} \quad (2)$$

$$\vec{B}_{\text{net},P} = \frac{\mu_0 i}{4\pi R_1} \frac{7\pi}{4} \hat{k} + \frac{\mu_0 i}{4\pi R_2} \frac{7\pi}{4} (-\hat{k})$$


$$= \frac{\mu_0 i}{16} \left(\frac{1}{R_1} - \frac{1}{R_2} \right) \hat{k}$$

$$\rightarrow |\vec{B}_{\text{net},P}| = \frac{7}{16} \left(4\pi \times 10^{-7} \frac{\text{Tm}}{\text{A}} \right) (0.2 \text{ A}) \left(\frac{1}{4} - \frac{1}{2} \right)$$

$$= 2.7 \times 10^{-8} \text{ T} \rightarrow \vec{B}_{\text{net},P} = 2.7 \times 10^{-8} \text{ T} (-\hat{k}) \quad \text{into the page}$$

(2) (2)

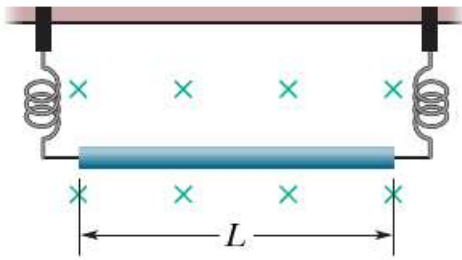4. A 13.0 g wire of length $L=62.0$ cm is suspended by a pair of flexible leads in a uniform magnetic field of magnitude 0.440 T (see Figure below).



What are the

i magnitude

ii direction (left or right, why?)

of the current required to remove the tension in the supporting leads?

Hint: Remove the tension means $\Sigma \vec{F}_{net} = 0 = \vec{F}_g + \vec{F}_B$

\vec{y}
 \vec{x}

suspension $\Rightarrow \Sigma \vec{F}_{net} = 0 = \vec{F}_g + \vec{F}_B$

$\uparrow iL\vec{B} = \vec{F}_B$
 $\downarrow mg = \vec{F}_g$

so that \vec{F}_B should be upward

i) $|\vec{F}_g| = |\vec{F}_B| \Rightarrow mg = iLBS \sin 90^\circ$

$\vec{F}_B \uparrow$
 $\vec{B} \rightarrow$
 $i \rightarrow$

$(5) i = \frac{mg}{LB} = \frac{(13.0 \times 10^{-3} \text{ kg})(9.8 \text{ m/s}^2)}{(0.620 \text{ m})(0.440 \text{ T})}$
 $= 0.467 \text{ A}$

ii) \vec{F}_B should be upward - so RHR \Rightarrow towards right

(3) (2) (5)

5. A uniform magnetic field B is perpendicular to the plane of a circular loop of diameter 10 cm formed from wire of diameter 2.5 mm and resistivity $1.69 \times 10^{-8} \Omega m$. At what rate must the magnitude of B change to induce a 10 A current in the loop?

$$R = \frac{V}{I} = \rho \frac{L}{A} = 1.69 \times 10^{-8} \Omega m \frac{\pi(0.10 m)}{\pi \left(\frac{2.5 \times 10^{-3} m}{2} \right)^2} = \frac{1.08 \times 10^{-3} \Omega}{(1)(1)}$$

where $L: 2\pi r$ & $A = \pi r^2$

$$\mathcal{E}_{ind} = \frac{d\Phi_B}{dt} = \frac{d(BA)}{dt} = A \frac{dB}{dt} \quad \& \quad i_{ind} = \frac{\mathcal{E}_{ind}}{R} \quad (1)$$

$$\Rightarrow i_{ind} R = A \frac{dB}{dt} \quad \Rightarrow \frac{dB}{dt} = \frac{i_{ind} R}{A} = \frac{i_{ind} R}{\pi r^2}$$

$$\Rightarrow \left| \frac{dB}{dt} \right| = \frac{(10 A)(1.08 \times 10^{-3} \Omega)}{\pi (0.10/2 m)^2} = \boxed{1.377 \text{ T/s}} \quad (2)(1)$$