

Halliday/Resnick/Walker Fundamentals of Physics

Classroom Response System Questions

Chapter 25 Capacitance

Interactive Lecture Questions

25.2.1. How much charge is on the plates of a 11- μ F capacitor that has been connected to a 120 V dc power supply for a long time?

a) 1.3×10^{-3} C

b) 9.2×10^{-2} C

c) 1.1×10^{-4} C

d) 1.3×10^{-6} C

e) 1.2×10^{-1} C

25.2.1. How much charge is on the plates of a 11- μF capacitor that has been connected to a 120 V dc power supply for a long time?

a) $1.3 \times 10^{-3} \text{ C}$

b) $9.2 \times 10^{-2} \text{ C}$

c) $1.1 \times 10^{-4} \text{ C}$

d) $1.3 \times 10^{-6} \text{ C}$

e) $1.2 \times 10^{-1} \text{ C}$

25.2.2. A $150\text{-}\mu\text{F}$ capacitor is fully-charged when it has $6.1 \times 10^{-3}\text{ C}$ on its plates. What is the potential difference across the plates of the capacitor?

- a) 250 V
- b) 41 V
- c) 0.0024 V
- d) 2.5 V
- e) 4.1 V

25.2.2. A $150\text{-}\mu\text{F}$ capacitor is fully-charged when it has $6.1 \times 10^{-3}\text{ C}$ on its plates. What is the potential difference across the plates of the capacitor?

a) 250 V

b) 41 V

c) 0.0024 V

d) 2.5 V

e) 4.1 V

- 25.4.1. Capacitor B has one-half the capacitance of capacitor A. How does the charge on capacitor A compare to that on B when the two are connected in series to a battery for a long time?
- a) The charge on capacitor A is one-fourth the charge on capacitor B.
 - b) The charge on capacitor A is one-half the charge on capacitor B.
 - c) The charge on capacitor A is the same as the charge on capacitor B.
 - d) The charge on capacitor A is twice the charge on capacitor B.
 - e) The charge on capacitor A is four times the charge on capacitor B.

25.4.1. Capacitor B has one-half the capacitance of capacitor A. How does the charge on capacitor A compare to that on B when the two are connected in series to a battery for a long time?

- a) The charge on capacitor A is one-fourth the charge on capacitor B.
- b) The charge on capacitor A is one-half the charge on capacitor B.
- c) The charge on capacitor A is the same as the charge on capacitor B.
- d) The charge on capacitor A is twice the charge on capacitor B.
- e) The charge on capacitor A is four times the charge on capacitor B.

25.4.2. Capacitor B has one-half the capacitance of capacitor A. How does the charge on capacitor A compare to that on B when the two are connected in parallel with a battery for a long time?

- a) The charge on capacitor A is one-fourth the charge on capacitor B.
- b) The charge on capacitor A is one-half the charge on capacitor B.
- c) The charge on capacitor A is the same as the charge on capacitor B.
- d) The charge on capacitor A is twice the charge on capacitor B.
- e) The charge on capacitor A is four times the charge on capacitor B.

25.4.2. Capacitor B has one-half the capacitance of capacitor A. How does the charge on capacitor A compare to that on B when the two are connected in parallel with a battery for a long time?

- a) The charge on capacitor A is one-fourth the charge on capacitor B.
- b) The charge on capacitor A is one-half the charge on capacitor B.
- c) The charge on capacitor A is the same as the charge on capacitor B.
- d) The charge on capacitor A is twice the charge on capacitor B.
- e) The charge on capacitor A is four times the charge on capacitor B.

25.4.4. Two parallel conducting plates are connected to a battery for a long time and become fully-charged. How does the potential difference across the plates change, if at all, when a conducting slab is inserted in between the plates without touching either plate?

- a) The potential difference will increase.
- b) The potential difference will decrease.
- c) The potential difference will remain unchanged.

25.4.4. Two parallel conducting plates are connected to a battery for a long time and become fully-charged. How does the potential difference across the plates change, if at all, when a conducting slab is inserted in between the plates without touching either plate?

- a) The potential difference will increase.
- b) The potential difference will decrease.
- c) The potential difference will remain unchanged.

25.4.5. Two parallel conducting plates are connected to a battery for a long time and become fully-charged. How does the charge on the plates change, if at all, when a conducting slab is inserted in between the plates without touching either plate?

- a) The charge will increase.
- b) The charge will decrease.
- c) The charge will remain unchanged.

25.4.5. Two parallel conducting plates are connected to a battery for a long time and become fully-charged. How does the charge on the plates change, if at all, when a conducting slab is inserted in between the plates without touching either plate?

- a) The charge will increase.
- b) The charge will decrease.
- c) The charge will remain unchanged.

25.4.7. Three parallel plate capacitors, each having a capacitance of $1.0 \mu\text{F}$ are connected in series. The potential difference across the combination is 100 V . What is the charge on any one of the capacitors?

a) $33 \mu\text{C}$

b) $330 \mu\text{C}$

c) $3300 \mu\text{C}$

d) $100 \mu\text{C}$

e) $1000 \mu\text{C}$

25.4.7. Three parallel plate capacitors, each having a capacitance of $1.0 \mu\text{F}$ are connected in series. The potential difference across the combination is 100 V . What is the charge on any one of the capacitors?

a) $33 \mu\text{C}$

b) $330 \mu\text{C}$

c) $3300 \mu\text{C}$

d) $100 \mu\text{C}$

e) $1000 \mu\text{C}$

25.5.1. The plates of an isolated parallel plate capacitor are separated by a distance d and carry charge of magnitude q . The distance between the plates is then reduced to $d/2$. How is the energy stored in the capacitor affected by this change?

- a) The energy increases to twice its initial value.
- b) The energy increases to four times its initial value.
- c) The energy is not affected by this change.
- d) The energy decreases to one fourth of its initial value.
- e) The energy decreases to one half of its initial value.

25.5.1. The plates of an isolated parallel plate capacitor are separated by a distance d and carry charge of magnitude q . The distance between the plates is then reduced to $d/2$. How is the energy stored in the capacitor affected by this change?

- a) The energy increases to twice its initial value.
- b) The energy increases to four times its initial value.
- c) The energy is not affected by this change.
- d) The energy decreases to one fourth of its initial value.
- e) The energy decreases to one half of its initial value.

25.6.4. Which one of the following changes will necessarily increase the capacitance of a capacitor?

- a) decreasing the charge on the plates
- b) increasing the charge on the plates
- c) placing a dielectric between the plates
- d) increasing the potential difference between the plates
- e) decreasing the potential difference between the plates

25.6.4. Which one of the following changes will necessarily increase the capacitance of a capacitor?

a) decreasing the charge on the plates

b) increasing the charge on the plates

c) placing a dielectric between the plates

d) increasing the potential difference between the plates

e) decreasing the potential difference between the plates

25.6.5. Complete the following statement: When a dielectric with constant κ is inserted between the plates of a charged *isolated* capacitor


- a) the capacitance is reduced by a factor κ .
- b) the charge on the plates is reduced by a factor of κ .
- c) the charge on the plates is increased by a factor of κ .
- d) the electric field between the plates is reduced by a factor of κ .
- e) the potential difference between the plates is increased by a factor of κ

25.6.5. Complete the following statement: When a dielectric with constant κ is inserted between the plates of a charged *isolated* capacitor

- a) the capacitance is reduced by a factor κ .
- b) the charge on the plates is reduced by a factor of κ .
- c) the charge on the plates is increased by a factor of κ .
- d) the electric field between the plates is reduced by a factor of κ .
- e) the potential difference between the plates is increased by a factor of κ

25.6.6. The figure shows four parallel plate capacitors: **A**, **B**, **C**, and **D**. Each capacitor carries the same charge Q and has the same plate area A . As suggested by the figure, the plates of capacitors **A** and **C** are separated by a distance d while those of **B** and **D** are separated by a distance $2d$. Capacitors **A** and **B** are maintained in vacuum while capacitors **C** and **D** contain dielectrics with constant $\kappa = 5$. Which of the following choices ranks the capacitors in order of increasing capacitance?

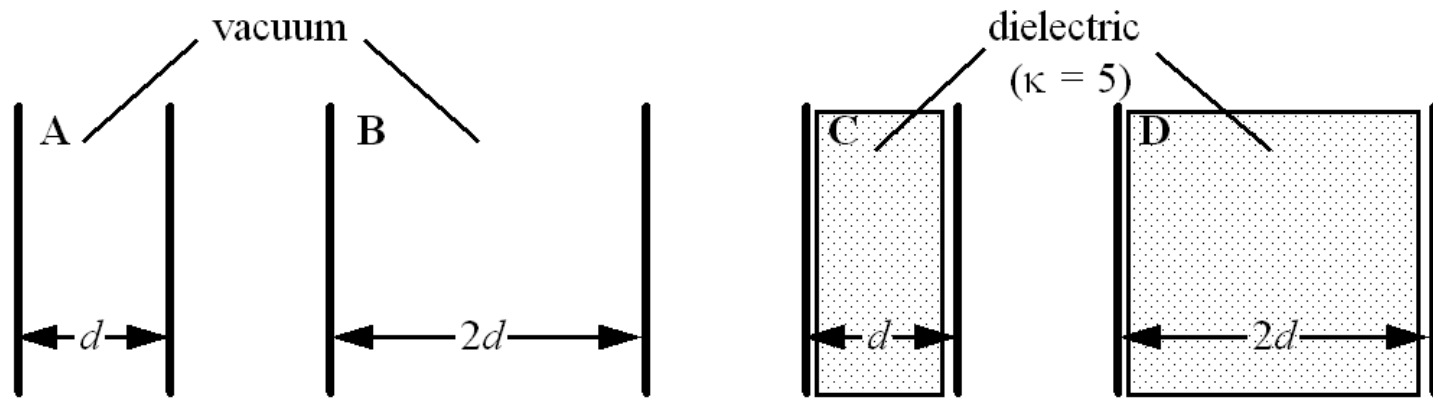- a) **A, B, C, D**
- b) **B, A, C, D**
- c) **A, B, D, C**
- d) **B, A, D, C**
- e) **D, C, B, A**



25.6.6. The figure shows four parallel plate capacitors: **A**, **B**, **C**, and **D**. Each capacitor carries the same charge Q and has the same plate area A . As suggested by the figure, the plates of capacitors **A** and **C** are separated by a distance d while those of **B** and **D** are separated by a distance $2d$. Capacitors **A** and **B** are maintained in vacuum while capacitors **C** and **D** contain dielectrics with constant $\kappa = 5$. Which of the following choices ranks the capacitors in order of increasing capacitance?

a) **A, B, C, D**

b) **B, A, C, D**

c) **A, B, D, C**

d) **B, A, D, C**

e) **D, C, B, A**

